

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.Tech. DEGREE EXAMINATION, NOVEMBER 2023
Sixth Semester

18EIC305T – POWER ELECTRONICS AND DRIVES
(For the candidates admitted from the academic year 2020-2021 to 2021-2022)

Note:

- (i) **Part - A** should be answered in OMR sheet within first 40 minutes and OMR sheet should be handed over to hall invigilator at the end of 40th minute.
- (ii) **Part - B & Part - C** should be answered in answer booklet.

Time: 3 hours

Max. Marks: 100

PART – A (20 × 1 = 20 Marks)

Answer **ALL** Questions

Marks BL CO PO

- | | | | | |
|---|---|---|---|---|
| 1. Identify the reverse recovery time for general purpose diode | 1 | 1 | 1 | 1 |
| (A) 20 μs | | | | |
| (B) 25 μs | | | | |
| (C) 30 μs | | | | |
| (D) 5 μs | | | | |
| 2. MOSFET is said to be _____ switch. | 1 | 1 | 1 | 1 |
| (A) Uncontrolled | | | | |
| (B) Semi controlled | | | | |
| (C) Fully controlled | | | | |
| (D) Semi uncontrolled | | | | |
| 3. Thyristor is considered to be semi controlled switch because | 1 | 1 | 1 | 1 |
| (A) It can be turned off but not on | | | | |
| (B) It conducts only during one-half cycle of an alternating current wave | | | | |
| (C) It can be turned on but not off | | | | |
| (D) It can be turned on only during one half cycle of an alternating voltage wave | | | | |
| 4. The controlling parameter in IGBT is the | 1 | 1 | 1 | 1 |
| (A) I _G | | | | |
| (B) V _{GE} | | | | |
| (C) I _C | | | | |
| (D) V _{CE} | | | | |
| 5. Identify the other name of class A commutation | 1 | 1 | 2 | 2 |
| (A) Self commutation | | | | |
| (B) Resonant commutation | | | | |
| (C) Natural commutation | | | | |
| (D) Impulse commutation | | | | |
| 6. The thyristor turn-off requires that the anode current | 1 | 1 | 2 | 2 |
| (A) Falls below the holding current | | | | |
| (B) Falls below the latching current | | | | |
| (C) Rises above the holding current | | | | |
| (D) Rises above the latching current | | | | |
| 7. Triggering the circuit is called as | 1 | 1 | 2 | 2 |
| (A) Turn-off method | | | | |
| (B) Turn-on method | | | | |
| (C) Commutation circuits | | | | |
| (D) Natural commutation circuit | | | | |

8. The pulse gating is not suitable of _____
 (A) R loads (B) RC loads
 (C) RL loads (D) It is suitable of every type of load
9. AC-DC conversion is called as _____
 (A) Chopper (B) Inverter
 (C) Rectifier (D) Cyclo converter
10. The frequency of ripple in the output voltage of a three phase controlled bridge rectifier depends on _____
 (A) Firing angle (B) Load inductance
 (C) Load resistance (D) Supply frequency
11. A dual converters has _____
 (A) Two full converters in series (B) Two half converters in series
 (C) Two full converter in anti-parallel (D) Two half converters in anti-parallel
12. Cyclo converters converts _____
 (A) DC-DC (B) DC-AC
 (C) AC-AC (D) AC-DC
13. In DC choppers, the waveforms for input and output voltages are represented as _____
 (A) Discontinuous, continuous (B) Both continuous
 (C) Both discontinuous (D) Continuous, discontinuous
14. A step-up chopper has V_s as the source voltage and α as the duty cycle. express the output voltage for this chopper is given by _____
 (A) $V_s(1+\alpha)$ (B) $V_s/(1-\alpha)$
 (C) $V_s(1-\alpha)$ (D) $V_s/(1+\alpha)$
15. VSI will have better performance if its _____
 (A) Load inductance is small and source inductance is large (B) Both load inductance and source inductance are small
 (C) Both load inductance and source inductance are large (D) Load inductance is large and source inductance is small
16. In case of the 120° mode of operation, _____ devices conduct at a time.
 (A) 2 (B) 3
 (C) 4 (D) 6
17. SMPS are based on the _____ principle.
 (A) Phase control (B) Integral control
 (C) Chopper (D) MOSFET
18. Static UPS requires _____
 (A) Only rectifier (B) Only inverter
 (C) Both inverter and rectifier (D) None of the mentioned

32. a. Analyze the operation of battery-operated vehicle and the design of charging and discharging of battery. 12 4 5 3

(OR)

- b. Illustrate the uninterruptible power supply with its different mode of operation. 12 4 5 3

* * * * *