

First and Second Semester

(For the candidates admitted during the academic year 2020 - 2021 & 2021 - 2022)

i. **Part - A** should be answered in OMR sheet within first 40 minutes and OMR sheet should be handed over to hall invigilator at the end of 40th minute.

ii. **Part - B** and **Part - C** should be answered in answer booklet.


Max. Marks: 100

Marks BL CO

Marks BL CO

- 1 2 1

- 1 3 1

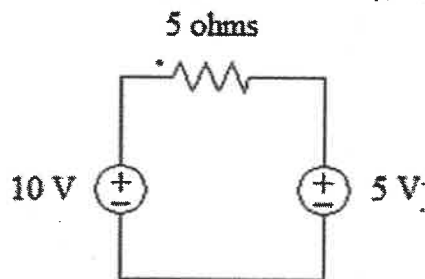

- (A) 1 A
(B) 2 A
(C) 3 A
(D) 5 A

- 1 2 1

- 1 1 1

- 1 1 2

- $$\begin{array}{ccc} 1 & 2 & 2 \end{array}$$

- 1 3 2


- | | | | |
|--|---|---|---|
| 8. Which of the following generators can build up the terminal voltage without any external source? | 1 | 1 | 2 |
| (A) Self-excited generator | | | |
| (B) Separately excited generator | | | |
| (C) Compound generator | | | |
| (D) Series generator | | | |
| 9. In a moving coil ammeter, the deflecting torque is directly proportional to | 1 | 1 | 3 |
| (A) Square of the current to be measured | | | |
| (B) Square root of the current to be measured | | | |
| (C) Current to be measured | | | |
| (D) Twice the current to be measured | | | |
| 10. A pointer of an instrument deflected and returns to zero position, when the current is removed is known as | 1 | 1 | 3 |
| (A) Damping Torques | | | |
| (B) Mass of the pointer | | | |
| (C) Controlling Torque | | | |
| (D) Action of gravity | | | |
| 11. The forward voltage drop across a silicon diode is about _____ | 1 | 2 | 3 |
| (A) 2.5 V | | | |
| (B) 3 V | | | |
| (C) 10 V | | | |
| (D) 0.7 V | | | |
| 12. Which circuit is used to cut the shape of output waveform? | 1 | 1 | 3 |
| (A) Clamper | | | |
| (B) Clipper | | | |
| (C) Peak amplifier | | | |
| (D) Sample and hold | | | |
| 13. In LVDT, when the iron core is exactly at center of tube then the net output of the transducer is | 1 | 2 | 4 |
| (A) Maximum | | | |
| (B) Average | | | |
| (C) Unpredictable | | | |
| (D) Zero | | | |
| 14. Photo diode will be generally connected in | 1 | 1 | 4 |
| (A) Forward bias | | | |
| (B) Reverse bias | | | |
| (C) No biasing required | | | |
| (D) Neutral | | | |
| 15. The property of light emitted from LASER is | 1 | 2 | 4 |
| (A) Polychromatic | | | |
| (B) Coherent | | | |
| (C) Not directional | | | |
| (D) Poor energy | | | |
| 16. A device is an adjustable resistor whose resistance differs inversely with the concentration of light | 1 | 2 | 5 |
| (A) Photo resistor | | | |
| (B) Thermistor | | | |
| (C) Photo transistor | | | |
| (D) Thermo couple | | | |
| 17. In Frequency Modulation the Amplitude of the Carrier Wave is | 1 | 2 | 5 |
| (A) Varies | | | |
| (B) Linearly Varies | | | |
| (C) Constant | | | |
| (D) Non-Linear | | | |
| 18. In FM wave the signal strength of each side band is determined by | 1 | 1 | 5 |
| (A) Modulation index | | | |
| (B) Bandwidth | | | |
| (C) Carrier wave | | | |
| (D) Power | | | |
| 19. The number of cells in 6 variable K-map is | 1 | 2 | 5 |
| (A) 4 | | | |
| (B) 16 | | | |
| (C) 32 | | | |
| (D) 64 | | | |
| 20. On a K-Map, grouping the 0s produces | 1 | 2 | 5 |
| (A) SOP expression | | | |
| (B) POS expression | | | |
| (C) A don't care condition | | | |
| (D) AND-OR expression | | | |

PART - B ($5 \times 4 = 20$ Marks)

Answer **any 5** Questions

Marks BL CO

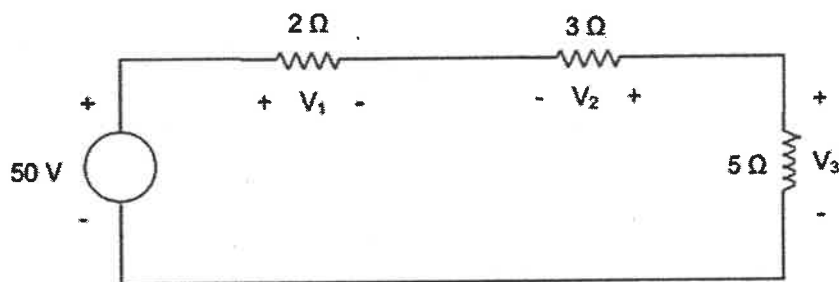21. For the circuit shown below find voltages V_1 , V_2 , and V_3 using Kirchhoff's voltage law. 4 3 1




22. Derive the relation between line voltage and phase voltage for a star-connected system. 4 2 1
23. A resistance of $100\ \Omega$ is connected in series with a 2 mH inductor to a supply at 230 V , 50 Hz . Determine current, power factor, and voltage across resistor and inductor. 4 3 2
24. Illustrate the operation of corridor wiring with its neat diagram. 4 1 3
25. Write short notes on photodiode. 4 2 4
26. Draw the block diagram of the communication system and explain the functions of each block. 4 2 5
27. Draw the logical diagram for the following expression. 4 2 5
 $Y = AC + AB + A\bar{B}C + AD + ACD$

PART - C ($5 \times 12 = 60$ Marks)

Answer all Questions


Marks BL CO

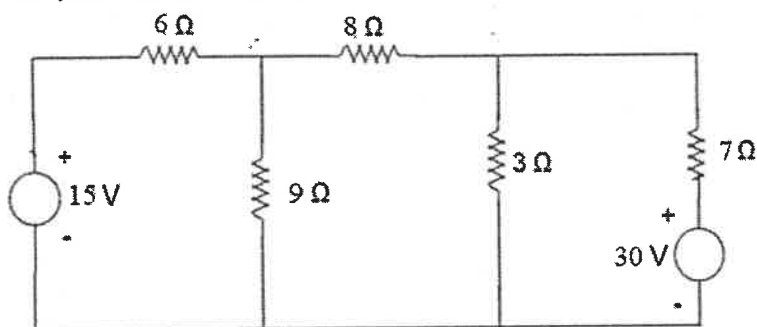28. (a) Find all the branch currents using Mesh analysis. Also find the power dissipated from $3\ \Omega$ resistor. 12 1 1



(OR)

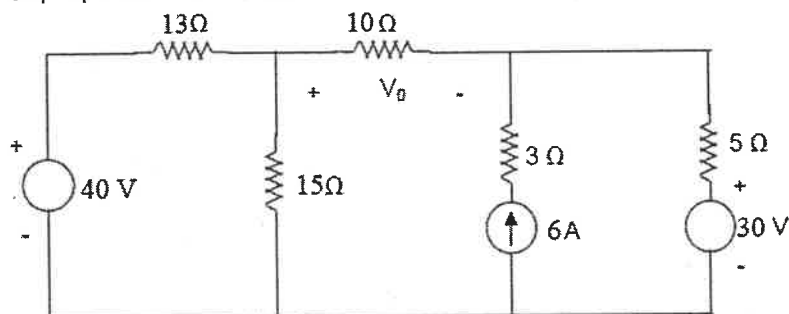- (b) Find the voltage response V_0 across the $10\ \Omega$ resistor using the Superposition theorem.



29. (a) With a neat diagram explain the construction and operation of a DC generator. 12 3 2

(OR)

- (b) (i). Analyse that the RMS and Average value of half-rectified sine wave are $\frac{I_m}{2}$ and $\frac{I_m}{\pi}$ respectively. [6 Marks]

(ii). A mild steel has a radius of 50 mm and a cross-sectional area of 400 mm². A current of 0.5 A flows in a coil wound uniformly around the ring and the flux produced is 0.1 mWb. If the relative permeability at this value of current is 200 A, find (I) the reluctance of the mild steel and (II) the number of turns in the coil. [6 Marks]

30. (a) Describe the construction and operation of a moving coil type of measuring instrument with a neat diagram. 12 2 3

(OR)

- (b) Interpret that $I_E = I_C + I_B$ in a BJT under CE configuration and also discuss the input and output characteristics with a neat diagram.

31. (a) Describe the construction and operation of LVDT with a neat diagram. Also justify that the output voltage is equal to the difference between the input voltages. 12 1 4

(OR)

- (b) With a neat diagram describe the construction and operation of the liquid crystal display system.

32. (a) (i) Simplify the following expression using Boolean algebra. 12 2 5

$$Y = \bar{A}BC\bar{D} + B\bar{C}\bar{D} + B\bar{C}D + B\bar{C}D \quad [6 \text{ Marks}]$$

- (ii) Simplify the given expression using K map.

$$Y(A,B,C) = \sum m(1,2,3,6,7) \quad [6 \text{ Marks}]$$

(OR)

- (b) What is meant by modulation? Also, explain the following with a neat diagram.

(i) Amplitude modulation [6 marks]

(ii) Frequency modulation [6 Marks]

* * * * *