

[illegible]

**B.Tech. DEGREE EXAMINATION, DECEMBER 2023**  
Fourth / Fifth Semester

18ECC202J – LINEAR INTEGRATED CIRCUITS  
(For the candidates admitted from the academic year 2020 - 2021)

**Note:**

- Note:**
- (i) **Part - A** should be answered in OMR sheet within first 40 minutes and OMR sheet should be handed over to hall invigilator at the end of 40<sup>th</sup> minute.
- (ii) **Part - B & Part - C** should be answered in answer booklet.

Time: 3 hours

Max. Marks: 100

**PART – A (20 × 1 = 20 Marks)**

### Answer ALL Questions

1. In 8-pin package of 741, terminals \_\_\_\_\_ and \_\_\_\_\_ used for dc offset. 1 1 1 1  
 (A) 1,5 (B) 2, 3  
 (C) 7,4 (D) 8, 6

2. Op-amp 741C has a low slew rate of 1 2 1 2  
 (A)  $0.6 \text{ V}/\mu\text{s}$  (B)  $0.5 \text{ V}/\mu\text{s}$   
 (C)  $00.5 \text{ mV}/\mu\text{s}$  (D)  $0.5\mu\text{V}/\mu\text{s}$

3. For 741C, CMRR is typically 1 1 2 1  
 (A) 80 dB (B) 70 dB  
 (C) 90 dB (D) 95 dB

4. The common-mode signal  $V_{cm}$  is defined as 1 2 2 2  
 (A)  $\frac{V_1 - V_2}{2}$  (B)  $V_1 + V_2$   
 (C)  $V_1 - V_2$  (D)  $\frac{V_1 + V_2}{2}$

5. An amplifier with a gain of +5, has  $R_1$  of  $5k\Omega$  and  $R_f$  of \_\_\_\_\_ 1 1 3 2  
 (A)  $20 \text{ k}\Omega$  (B)  $10 \text{ k}\Omega$   
 (C)  $15 \text{ k}\Omega$  (D)  $5 \text{ k}\Omega$

6. Another name for a unity gain amplifier is 1 1 2 3  
 (A) Difference amplifier (B) Comparator  
 (C) Single ended (D) Voltage follower

7. A circuit whose output is proportional to the difference between the input signals is considered to be which type of amplifier? 1 1 2 2  
 (A) Common mode (B) Darlington  
 (C) Differential (D) Operational

8. If the input to a comparator is a sine wave, the output is 1 2 2 3  
 (A) Ramp voltage (B) Sine wave  
 (C) Rectangular wave (D) Sawtooth wave
9. In the design of RC phase shift oscillator to generate 100 Hz signal, if  $C = 0.01\mu F$ , then R is 1 2 3 1  
 (A) 64.9 k $\Omega$  (B) 6.49 k $\Omega$   
 (C) 649  $\Omega$  (D) 64.9  $\Omega$
10. Which among the following can be used to detect the missing heart beat? 1 2 3 2  
 (A) Monostable multivibrator (B) Astable multivibrator  
 (C) Schmitt trigger (D) Comparator
11. The signal \_\_\_\_\_ shifts the VCO frequency in a direction to reduce 1 3 3 1  
 the frequency between  $f_s$  and  $f_0$ .  
 (A)  $V_s$  (B)  $V_e$   
 (C)  $V_c$  (D)  $V_0$
12. PLL is used in 1 2 3 1  
 (A) AM detection (B) QAM  
 (C) BPSK (D) QPSK
13. In which filter the output and input voltages are equal in amplitude for all 1 1 4 2  
 frequencies?  
 (A) All pass filter (B) Low pass filter  
 (C) High pass filter (D) Band pass filter
14. Name the filter that has two pass bands 1 2 4 2  
 (A) Band pass filter (B) Low pass filter  
 (C) High pass filter (D) Band reject filter
15. What is the dropout voltage in a 3 terminals IC regulators? 1 3 4 1  
 (A)  $|V_{in}| \geq |V_0| + 2V$  (B)  $|V_{in}| < |V_0| - 2V$   
 (C)  $|V_{in}| = |V_0|$  (D)  $|V_{in}| < |V_0|$
16. The % load regulation of a power supply is ideally \_\_\_\_\_ and 1 3 4 2  
 practically \_\_\_\_\_.  
 (A) Zero, small (B) Small, zero  
 (C) Zero, large (D) Large, zero
17. A monotonic DAC is one whose analog output increases for 1 1 5 2  
 \_\_\_\_\_  
 (A) Decrease in digital input (B) An increase in analog input  
 (C) An increase in digital input (D) Decrease in analog input
18. Find the resolution of a 10-bit ADC for an input range of 10 V. 1 1 4 3  
 (A) 97.7 mV (B) 9.77 mV  
 (C) 0.977 mV (D) 977 mV

19. Which ADC is considered to be simplest, fastest and most expensive? 1 1 4 2  
 (A) Servo tracking (B) Counter type  
 (C) Flash type (D) Successive approximation
20. Successive approximation type ADC completes n-bit conversion in 1 1 4 3  
 \_\_\_\_\_ clock periods.  
 (A)  $2^n - 1$  (B) 1  
 (C)  $n$  (D)  $2^n + 1$

**PART – B (5 × 4 = 20 Marks)**

Answer ANY FIVE Questions

- |  | Marks | BL | CO | PO |
|--|-------|----|----|----|
| 21. List the characteristics of an ideal op-amp. Give practical values.  | 4     | 2  | 1  | 3  |
| 22. Draw the block schematic of an op-amp and explain.   | 4     | 3  | 2  | 1  |
| 23. Draw the circuit of a transconductance amplifier and explain the operation.  | 4     | 2  | 3  | 2  |
| 24. Design an adder circuit using an op-amp to get output expression as $V_0 = -(0.5V_1 + V_2 + 15V_3)$ . Where $V_1, V_2$ and $V_3$ are the inputs. | 4     | 3  | 3  | 1  |
| 25. State the two condition of oscillation.  | 4     | 3  | 4  | 2  |
| 26. Draw the basic structure of feedback oscillator.   | 4     | 3  | 4  | 1  |
| 27. Write short notes on switched capacitor filter.  | 4     | 4  | 4  | 2  |

**PART – C (5 × 12 = 60 Marks)**

Answer ALL Questions

- |  | Marks | BL | CO | PO |
|--|-------|----|----|----|
| 28. a. List the non-ideal DC characteristics of an op-amp. Explain them.   | 12    | 3  | 1  | 4  |
| (OR)   |       |    |    |    |
| b.i. List the frequency compensation techniques. Explain any one.  | 6     | 2  | 1  | 3  |
| ii. For the non-inverting amplifier, $R_1 = 1k\Omega$ and $R_f = 10k\Omega$ . Calculate the maximum output offset voltage due to $V_{ios}$ and $I_B$ . The op-amp is LM307 with $V_{ios} = 10mV$ and $I_B = 300nA, I_{os} = 50nA$ . Calculate the value of $R_{comp}$ needed to reduce the effect of $I_B$ . Calculate the maximum output offset voltage of $R_{comp}$ is connected. | 6     | 3  | 2  | 1  |
| 29. a. List the important features of instrumentation amplifier. Explain the operation of instrumentation amplifier with neat diagram.   | 12    | 3  | 2  | 1  |
| (OR)   |       |    |    |    |
| b. Draw the circuit of a log amplifier and explain its operation with derivation of output.  | 12    | 3  | 2  | 1  |
| 30. a. With relevant diagram, explain the operation of triangular wave generator.  | 12    | 3  | 3  | 1  |

(OR)

- b.i. Derive the expression of time delay of monostable multivibrator using 555 timer. 8 3 3 1
- ii. In the astable multivibrator using 555 timer if  $R_A = 4.7k\Omega$ ,  $R_B = 1.5k\Omega$  and  $C = 0.1\mu F$ . Calculate  $t_{HIGH}$ ,  $t_{LOW}$ , free running frequency and duty cycle D. 4 3 3 1
31. a.i. With a neat diagram, explain the operation of narrow band pass filter. 8 4 3 1
- ii. Design a wide-band pass filter having  $f_l = 400Hz$ ,  $f_h = 2kHz$  and passband gain of 4. Find the value of Q of the filter. 4 4 3 1
- (OR)**
- b.i. What are the limitations of three terminal regulator? 2 3 2 4
- ii. Draw the functional diagram of 723 regulator and explain. 10 3 2 4
32. a. Explain the operation of R-2R ladder DAC with neat diagram. 12 3 4 3
- (OR)**
- b. With relevant diagrams explain the operation of ramp type ADC. 12 3 4 3

\* \* \* \* \*