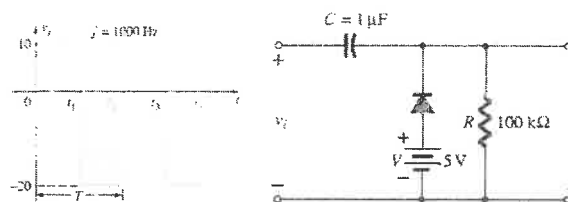


9. If the base-emitter voltage of the silicon BJT is 0.6V, what is the operating region of the BJT? 1 2 3
 (A) Break down (B) Cut off
 (C) Saturation (D) Active
10. If V_{BE} voltage of the BJT is 0.2V and $V_{CC} = 5V$ in CE configuration, What is the output of the transistor? (Assume the transistor is acting as a switch) 1 2 3
 (A) 0.2V (B) 5V
 (C) 1V (D) 0.5V
11. Recall, the relation between β and α 1 1 3
 (A) $\beta = 1 / (1 - \alpha)$ (B) $\beta = (1 - \alpha) / \alpha$
 (C) $\beta = \alpha / (1 - \alpha)$ (D) $\beta = \alpha / (1 + \alpha)$
12. Choose the phase difference between the input and output voltages in a common base configuration 1 1 3
 (A) 180 degree (B) 90 degree
 (C) 0 degree (D) 270 degree
13. Recall, the characteristics of MOSFET are ----- 1 1 4
 (A) Input and output characteristics (B) Drain and transfer characteristics
 (C) VI characteristics (D) Gate characteristics
14. What is CMOS? 1 1 4
 (A) Complementary metal oxide field effect transistor (B) Continuous metal oxide field effect transistor
 (C) Collector metal oxide field effect transistor (D) Curved metal oxide field effect transistor
15. At $V_{GS} = 0$, what happens to the channel of Depletion MOSFETs? 1 1 4
 (A) Conduct (B) Doesn't conduct
 (C) Rarely conduct (D) Insulate
16. A Halfwave rectifier is equivalent to 1 1 5
 (A) Clamper circuit (B) Clamper circuit with negative bias
 (C) Clamper circuit with positive bias (D) Clipper circuit
17. Determine v_o for the following network with the input shown (for ideal diode) 1 2 5



- (A) 0V (B) 1V
 (C) 2V (D) 5V
18. what is the efficiency of half wave rectifier 1 1 5
 (A) 80% (B) 40%
 (C) 20% (D) 10%
19. How many MOSFETs are necessary to make a NOT gate 1 2 5
 (A) 1 (B) 2
 (C) 3 (D) 4
20. The most popular type of ICs are----- 1 1 5
 (A) Thin film (B) Thick film
 (C) Hybrid (D) Monolithic

PART - B (5 × 4 = 20 Marks)Answer **any 5** Questions


Marks BL CO

- | | | | |
|--|---|---|---|
| 21. Derive the drift and diffusion current density of PN junction diode | 4 | 2 | 1 |
| 22. Explain Fermi Dirac function of semiconductor | 4 | 1 | 1 |
| 23. Calculate the capacitance of a varactor diode when it is reverse-biased with a voltage of 6V. The varactor diode has a capacitance-voltage (C-V) curve with a slope (k) of 20 pF/V | 4 | 2 | 2 |
| 24. What is negative resistance property? Relate this property with a high frequency diode | 4 | 1 | 2 |
| 25. Draw the three configurations of BJT | 4 | 1 | 3 |
| 26. Derive drain current of E MOSFET | 4 | 1 | 4 |
| 27. Write the applications of integrated circuits | 4 | 1 | 5 |

PART - C (5 × 12 = 60 Marks)Answer **all** Questions

Marks BL CO


- | | | | |
|---|----|---|---|
| 28. (a) (i) A silicon semiconductor at room temperature (300 K) as an intrinsic carrier concentration of $1.5 \times 10^{16} \text{ cm}^{-3}$. If it is doped with $2 \times 10^{18} \text{ cm}^{-3}$ phosphorus atoms, calculate the electron concentration and hole concentration at this temperature
(II) Explain the voltage rectification characteristics of PN junction diode
(OR)
(b) Explain the construction and VI Characteristics of Zener diode | 12 | 3 | 1 |
| 29. (a) Explain the following diodes
(i) Laser (ii) PIN Photodiode
(OR)
(b) Discuss the variable capacitance property of the Varactor diode | 12 | 2 | 2 |
| 30. (a) For the circuit shown below, the measurement indicates that $V_B = -1.5\text{V}$. Calculate V_E , α , β and V_C . If the transistor β value is infinity, what value of V_b , V_c and V_E in result? ($V_{BE} = 0.7\text{V}$) | 12 | 3 | 3 |

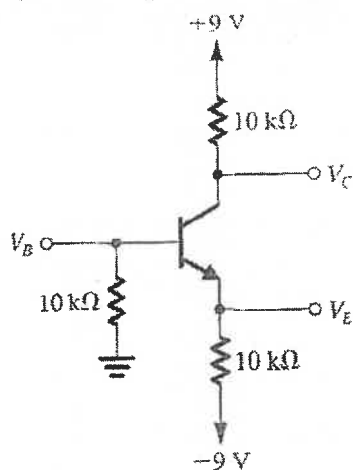

(OR)

- (b) Draw the hybrid Pi model of the transistor under CB configuration and explain the four parameters

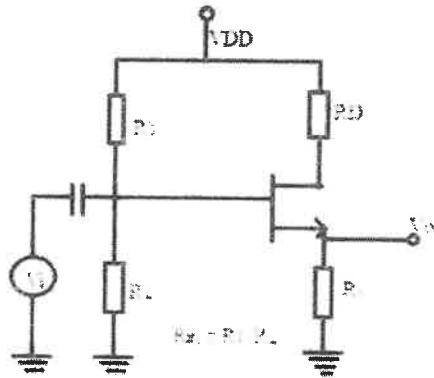31. (a) The following CD MOSFET amplifier circuit includes voltage divider bias, the two resistors like $R_1 = 2.5 \text{ M Ohm}$ & $R_2 = 1.5 \text{ M Ohm}$ respectively, then what is the R_{in} value? 12 2 4



(OR)

- (b) (i) Compare BJT and MOSFET
(ii) Discuss the configurations of PMOSFET and NMOSFET
32. (a) Briefly explain zener diode voltage regulators 12 1 5
- (OR)
- (b) Explain the following
(i) Diode clampers (ii) Diode multipliers

* * * * *