

**B.Tech DEGREE EXAMINATION, DECEMBER 2023**

Fourth and Fifth Semester

**18ECC202J - LINEAR INTEGRATED CIRCUITS**

(For the candidates admitted during the academic year 2018-19 to 2021-22)

**OPEN BOOK EXAMINATION****Note:**

- Specific approved THREE text books (Printed or photocopy) recommended for the course.
- Handwritten class notes (certified by the faculty handling the course / Head of the Department).

**Time: 3 Hours****Max. Marks: 100**Answer **FIVE** Questions

Marks BL

CO


(Question No. 1 is compulsory)

- 1 i. a. The input offset current compensated inverting amplifier shown in below figure. Determine the value of resistor  $R_4$  in the feedback network of an amplifier to provide the voltage gain of -120 [9 Marks]


18

4

1

 

- b. Explain the function of the circuit shown in Figure 1 and derive the output expression. Also, find the value of (i) input resistance (ii) voltage gain (iii) output voltage, where  $R_1=R_3=560\Omega$ ,  $R_f=R_2=5.6k\Omega$ ,  $V_1=2V$  (peak to peak),  $V_2=1V$  (peak to peak),  $R_i=2M\Omega$  and open loop gain  $A_{OL}=200000$ . [ 9 Marks]

 
**Figure 1**

- What will be the emitter current in a differential amplifier, where both the transistor are biased and matched? (Assume current to be  $I_Q$ )
 




(A) $I_E = I_Q/2$	(B) $I_E = I_Q$	1	1	1
(C) $I_E = (I_Q)^2/2$	(D) $I_E = (I_Q)^2$			
- A differential amplifier has a transistor with  $\beta_0 = 100$ , is biased at  $I_{CQ} = 0.48mA$ . Determine the value of CMRR and  $A_{CM}$ , if  $R_E = 7.89k\Omega$  and  $R_C = 5k\Omega$ .
 

(A) 49.54 db	(B) 49.65 db	1	1	1
(C) 49.77 db	(D) 49.60 db			

 
2. i. Analyze the function of the circuit shown in the Figure and derive its output voltage. Also, calculate the output voltage, where  $V_1=2V$ ,  $V_2=5V$ ,  $V_3=3V$ ,  $V_4=1V$ ,  $V_5=3V$ ,  $V_6=2V$ . Assume that the op-amp is initially nulled. 18 4 2



   - ii. What happens if the potentiometer  $R_p$  (10 k Ohms) is connected to negative supply? 1 1 2



- iii. How to minimize the response time and increase the operating frequency range of the op-amp? 1 1 2
- (A) Positive halfwave rectifier with two diodes (B) Positive halfwave rectifier with one diode
- (C) Negative halfwave rectifier with two diodes (D) Negative halfwave rectifier with one diode
- 3 i. a. Design a circuit using 555 timer, which will flash the electric bulb such that it's ON time will be 3 seconds and OFF time will be 1 second. [ 9 Marks] 18 4 3
- b. Find the phase error necessary to produce a VCO frequency shift of  $\Delta f = 10$  KHz for an open loop gain of  $KV = 40$  KHz/rad. What will be the deviation of phase error if  $\Delta f$  shifts to 5 KHz? [ 9 Marks]

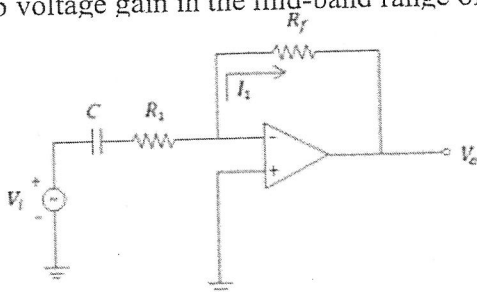- ii. How to achieve 50% duty cycle in adjustable rectangular wave generator? (Assume  $R_1 \rightarrow$  Resistor connected between supply and discharge and  $R_2 \rightarrow$  Resistor connected between discharge and trigger input.) 1 1 3  
 (A)  $R_1 < R_2$  (B)  $R_1 > R_2$   
 (C)  $R_1 = R_2$  (D)  $R_1 \geq R_2$
- iii. A basic feedback oscillator is satisfying the Barkhausen criterion. If the  $\beta$  value is given as 0.7072, find the gain of basic amplifier? 1 1 3  
 (A) 2.1216 (B) 0.7072  
 (C) 1 (D) 1.414
- 4 i. a. Design an active low pass filter with a gain of 4, a corner frequency of 1 kHz, and a gain roll-off rate of -60 dB/decade. [9 Marks] 18 3 4  
 b. Design an active high pass filter with a gain of 10, a corner frequency of 2 kHz, and a gain roll-off rate of 40 dB/decade. [9 Marks]
- ii. Find the High cut-off frequency if the pass band gain of a filter is 10. 1 1 4  
 (A) 70.7 Hz (B) 7.07 KHz  
 (C) 7.07 Hz (D) 707 Hz
- iii. What happens if inductors are used in low frequency applications? 1 1 4  
 (A) Enhance inductor usage (B) No losses occurs  
 (C) Degrades inductor performance (D) Low power dissipation
- 5 i. a. "An ADC which uses a very efficient code search strategy to complete n-bit conversion in just n-clock periods" - Identity a suitable ADC that will fulfill this statement and explain with an example how the input analog signal will be converted to digital output signal. [10 Marks] 18 3 5  
 b. A basic step of 8-Bit DAC has a resolution of 10 mV. Find the corresponding analog output voltage for the inputs 10101100.
- ii. The smallest resistor in a 12 bit weighted resistor DAC is 2.5k $\Omega$ , what will be the largest resistor value? 1 1 5  
 (A) 40.96M $\Omega$  (B) 10.24M $\Omega$   
 (C) 61.44 M $\Omega$  (D) 18.43M $\Omega$
- iii. Find out the resolution of 8 bit DAC/ADC? 1 1 5  
 (A) 562 (B) 625  
 (C) 256 (D) 265
- 6 i. a. The drift parameter of an operational amplifier used in a non-inverting amplifier is given below. 18 3 2  
 Input offset voltage variation =  $\pm 12 \mu\text{V}/^\circ\text{C}$  Input offset current variation =  $\pm 0.4 \text{ nA}/^\circ\text{C}$   
 Assuming  $R_f = 1.3 \text{ M}\Omega$  and  $R_i = 150 \text{ K}\Omega$  and output  $V_o = 0 \text{ V}$  at  $25^\circ\text{C}$ , find the output voltage at  $60^\circ\text{C}$  due to offset voltage variation and due to offset current variation. [9 Marks]
- b. In the inverting AC amplifier circuit shown in Fig. below,  $V_i = 2 \text{ V}$ ,  $C = 0.1 \mu\text{F}$ ,  $R_1 = 15 \text{ K}\Omega$ , and  $R_f = 150 \text{ K}\Omega$ . Calculate the lower 3dB frequency and the approximate closed-loop voltage gain in the mid-band range of frequencies. [9 Marks]
- 
- ii. How many equal intervals are present in a 14-bit D-A converter? 1 1 2  
 (A) 16383 (B) 4095  
 (C) 65535 (D) 1023

- iii. How an AC amplifier can be powered by a single supply voltage, produces voltage swing? 1 1 2
- (A) By inserting a voltage divider at the inverting input (B) By inserting a voltage divider at the non-inverting input
- (C) By inserting a voltage divider at the output (D) By inserting a voltage divider at the feedback circuit
- 7 i. If an analog input of 8.3 V is given as an input to a 4 bit SAR ADC, illustrate the conversion code search sequence for a clock frequency of 100 Hz. Complete step by step search flow diagram starting from MSB with the block diagram of the 4 bit SAR ADC must be provided. Also if the full scale analog voltage is 15 V, provide the Digital VS Analog conversion chart with your assumed quantization level. 18 4 3
- ii. Find the error voltage of phase comparator, whose input signal is  $V_s = V_s \sin(2\pi f_s t)$  and the output signal  $V_o = V_o \sin(2\pi f_o t + \phi)$ . 1 1 3
- (A)  $V_e = [k \times (V_s/2)] \times [\cos(-\phi) - \cos(2\pi f_o t + \phi)]$  (B)  $V_e = [k \times V_s \times (V_o/2)] \times [\cos(-\phi) - \cos(2\pi f_o t + \phi)]$
- (C)  $V_e = [k \times V_s \times (V_o/2)] \times [\cos(-\phi) + \cos(2\pi f_o t + \phi)]$  (D)  $V_e = [k \times V_s \times V_o] \times [\cos(-\phi) - \cos(2\pi f_o t + \phi)]$
- iii. Calculate the value of external timing capacitor, if no modulating input signal is applied to VCO. Consider  $f_o = 25$  kHz and  $R_T = 5$  k $\Omega$ . 1 1 3
- (A) 6nF (B) 100 $\mu$ F
- (C) 2nF (D) 10nF

\* \* \* \* \*